

CSE360- Computer Interfacing
Quiz 03; Spring'26
Set B

Name: _____ ID: _____ Section: _____

Marks: 15 points

Time: 20 minutes

Instructions: Answer all questions on the space provided below for each.

Question 1 (CO2 - 15 points): An 82C55 IC's Port A is connected to a Keyboard, port B is connected to a monitor and two LEDs are supposed to be connected in port C.

a. Draw the configuration diagram for the above scenario. [4]


b. Write down the control bits for the above scenario. [3]

1011x10x → two LEDs are still not connected
1011010x → " " " connected to PC6, PC7.
10110100 → " " " " to PC0, PC6, PC7.

c. Mention which pins of port C will be used to connect the LEDs in the system? [2]

PC0, PC6, PC7. any two.

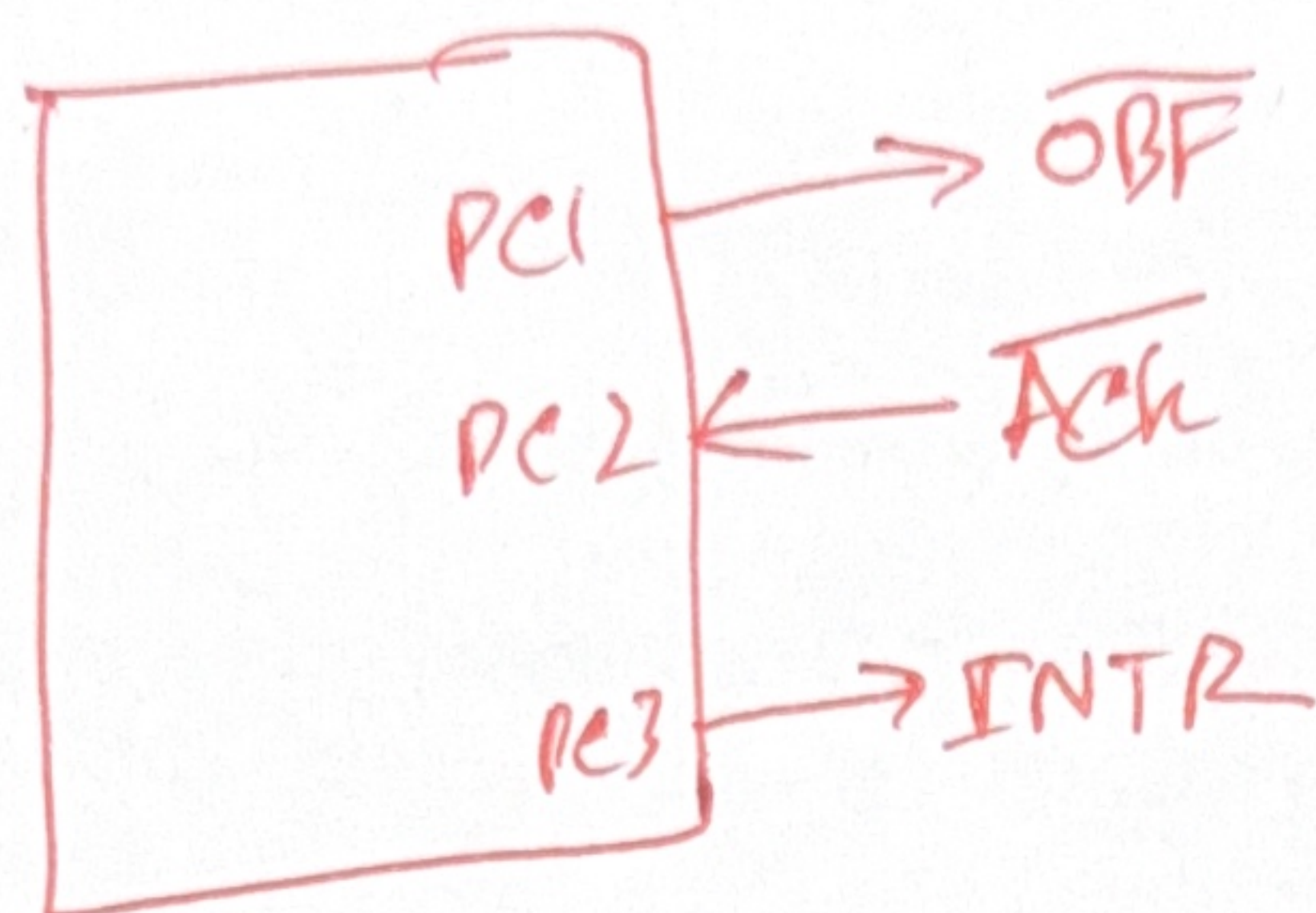- d. Draw the handshaking diagram of port B only for the given scenario with appropriate pin numbers and signal labeling and explain the handshaking process. [6]



port B

output handshaking.

then timing diagram.

bit 7 to bit 0 ← 1011101
 bit 7 to bit 0 ← 1011010
 bit 7 to bit 0 ← 00101101

ack. pin